

EXPERIMENT-6

MEASUREMENT OF CAPACITANCE BY SCHERING BRIDGE

AIM:

- To Determine the Capacitance of an unknown Capacitor.

THEORY:

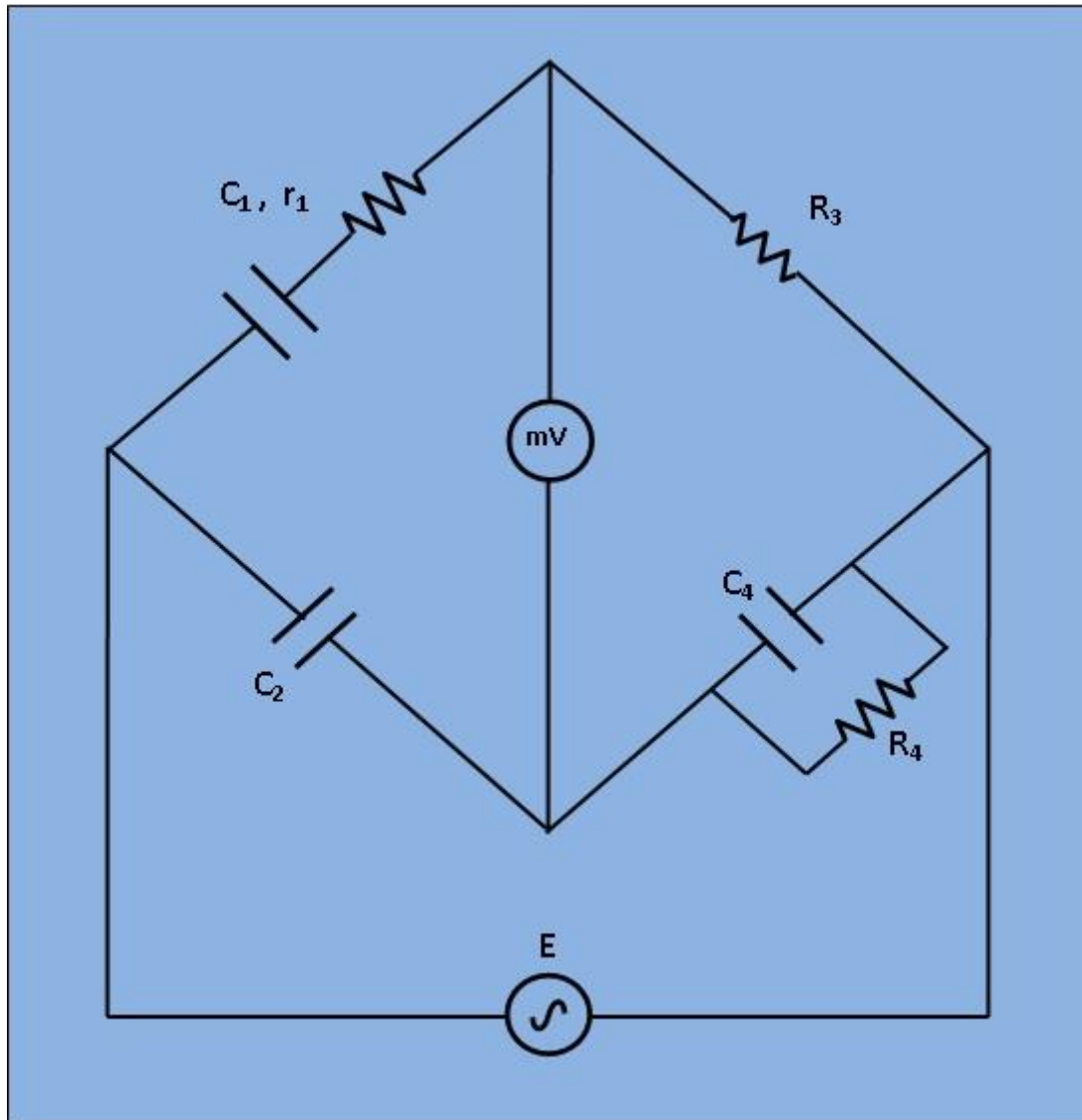


Fig 1: Circuit diagram for measurement of Capacitance by Schering Bridge

Let,

C_1 =capacitor whose capacitance is to be measured.

r_1 = a series resistance representing the loss in the capacitor C_1 .

C_2 = a standard capacitor.

R_3 = a non inductive resistance.

C_4 = a variable capacitor.

R_4 = a variable non inductive resistance.

At balance,

$$\left(r_1 + \frac{1}{j\omega C_1}\right) * \left(\frac{R_4}{j\omega C_4 R_4 + 1}\right) = \frac{R_3}{j\omega C_2} \dots\dots (1)$$

$$r_1 R_4 - \frac{jR_4}{\omega C_1} = -\frac{jR_3}{\omega C_2} + \frac{R_3 R_4 C_4}{C_2} \dots\dots (2)$$

Or Equating the real and imaginary terms in equa. (2), we obtain

$$r_1 = R_3 * \frac{C_4}{C_2} \dots\dots (3)$$

$$C_1 = R_4 * \frac{C_2}{R_3} \dots\dots (4)$$

And, Two independent balance equations (3) and (4) are obtained if C_4 and R_4 are chosen as the variable elements.

Dissipation factor

$$D_1 = \omega C_1 r_1 \dots\dots (5)$$

PROCEDURE:


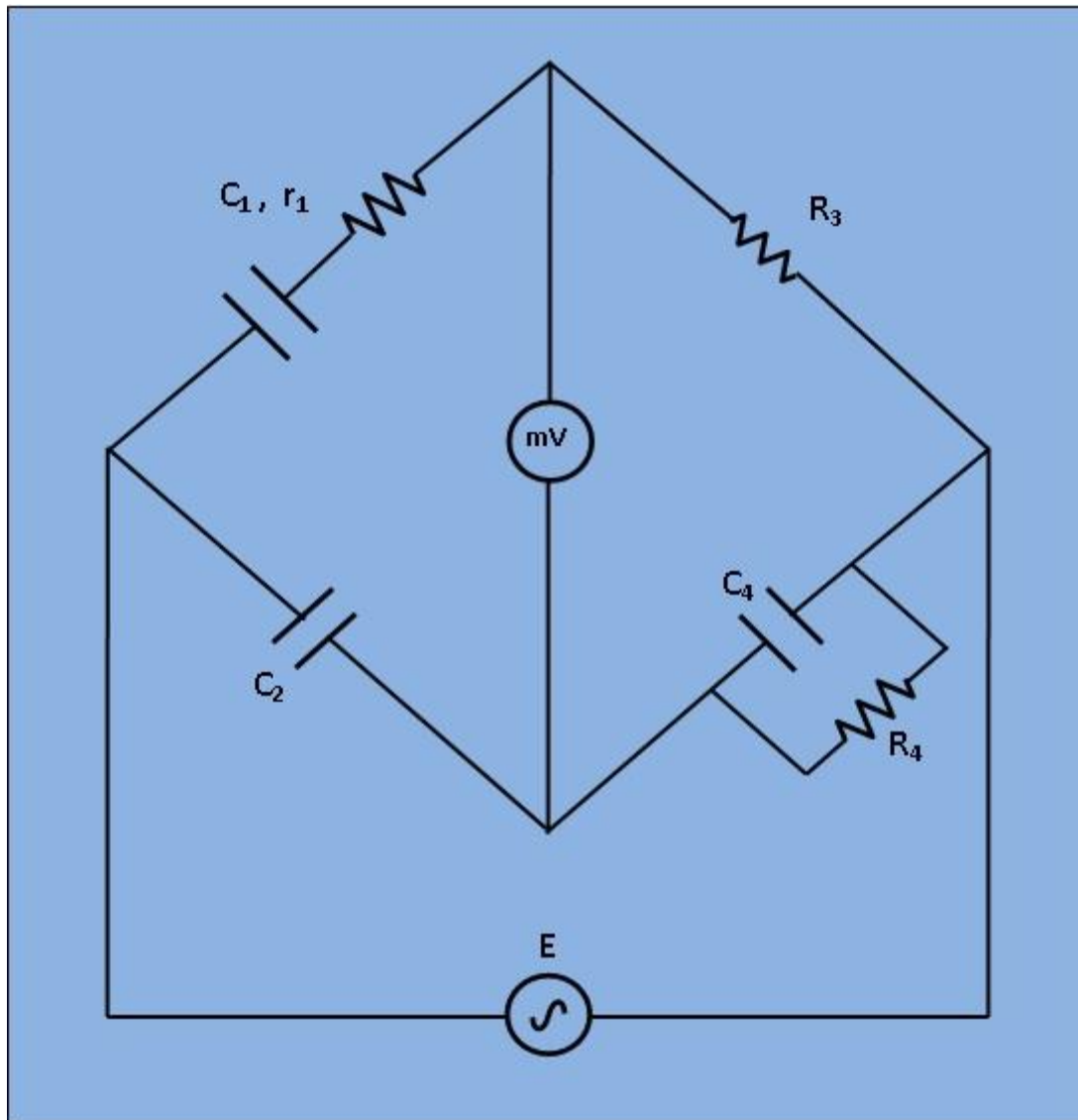


Fig. 1. Circuit diagram of experimental set-up for Capacitance measurement by Schering Bridge.

- 1) Apply Supply voltage from the signal generator with arbitrary frequency. ($V = 3\text{V}$). Also set the unknown Capacitance value from 'Set Capacitor Value' tab
- 2) Then switch on the supply to get millivoltmeter deflection.
- 3) Choose the values of C_2 , C_4 , R_3 and R_4 from the capacitance and resistance box. Vary the values to some particular values to achieve "NULL".
- 4) Observe the millivoltmeter pointer to achieve "NULL".
- 5) If "NULL" is achieved, switch to 'Measure Capacitor Value' tab and click on 'Simulate'. Observe the calculated values of unknown capacitance (C_1) and its internal resistance (r_1).
- 6) Also observe the Dissipation factor of the unknown capacitor which is defined as

$$\omega * C * r \text{ Where, } \omega = 2\pi f$$

SIMULATION:

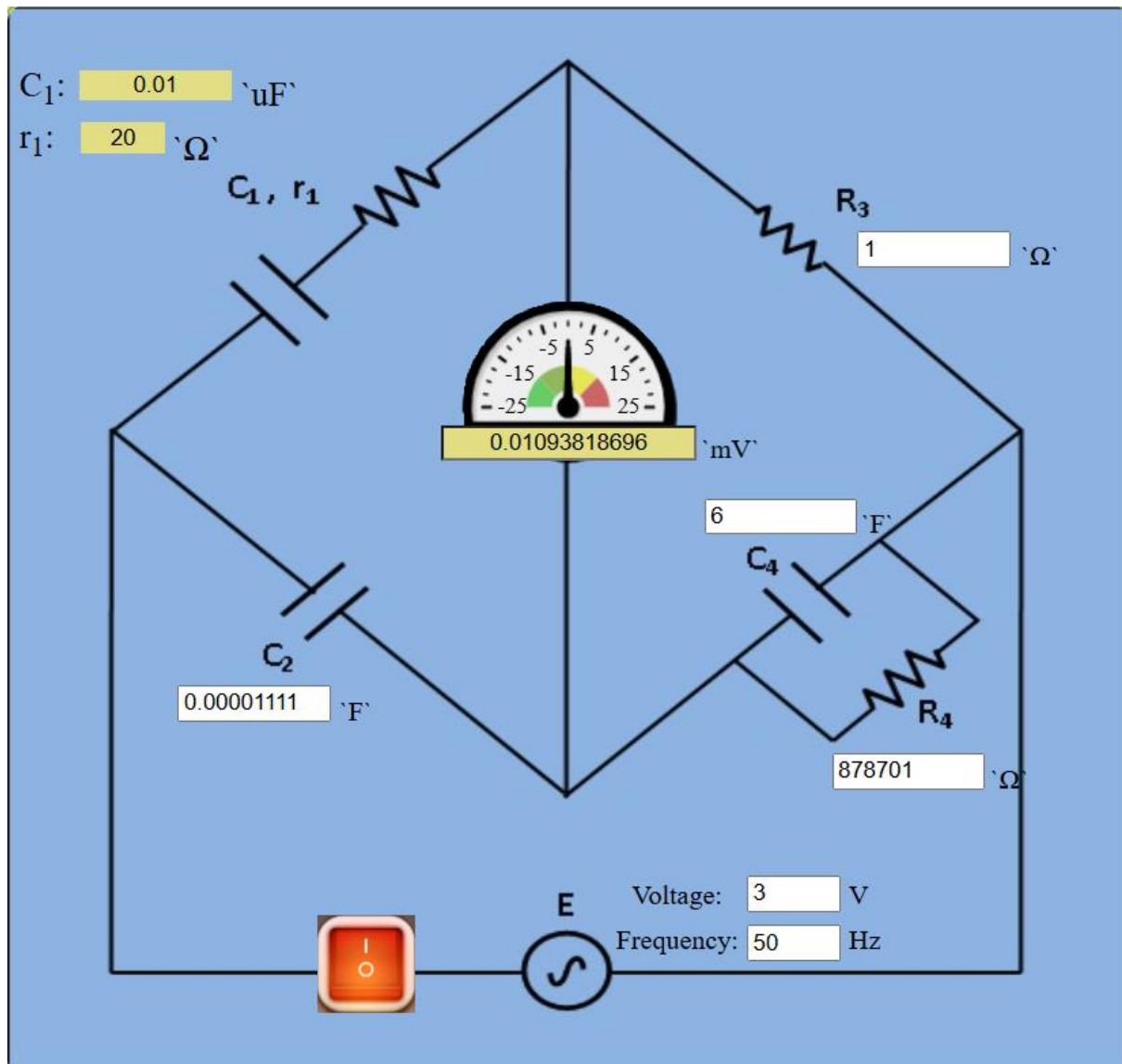

CONTROLS			
R3 : 1 Ω	<input type="range"/>		11.11111 $\text{M}\Omega$
R4 : 1 Ω	<input type="range"/>		11.11111 $\text{M}\Omega$
C2 : 100 pF	<input type="range"/>		11.111 μF
C4 : 100 pF	<input type="range"/>		11.111 μF

MEASURE CAPACITOR VALUE:

The current voltmeter reading is: 0.0109381869 mv. Now simulate to get:

Capacitor value (in μF): 9.7624e+6

Resistance value (in Ω): 5.4005e+5

Dissipation Factor: 1.6555e+9

Simulate

RESULT:

Thus , the unknown capacitance is found using schering bridge.